

# Detachable-Keys-Piano

- By Rohit Dattatreya Hegde (<https://github.com/ROHITDH/Detachable-Keys-Piano>)
- For a quick demo: <https://www.youtube.com/watch?v=aoMrV8k0poE>

## **Table of Contents:**

- ABSTRACT
- METHODOLOGY
- THEORY
- DESIGN AND IMPLEMENTATION
- DEMO
- DOWNLOAD
- ABOUT TOOLS USED
- ACKNOWLEDGEMENT

## **1. ABSTRACT**

Like all other fields, technology plays a crucial role in the musical world. The piano is one of the undetachable members of this world that has to improve for the dynamic growth of the field. But its abiding nature, difficulties in portability, and increasing demand for the interconnection along with the virtual world (digital media) have given space for technophiles to develop. 'DETACHABLE PIANO KEYS WITH DUPLEX TUTOR' is an instrument that overcomes all these limitations by providing a set of keys that can be attached or detached as per the requirement of the user. So that the same instrument can cover a domain ranging from the novice to the trained and experienced musicians. The number of keys is decided by the user as per their requirement so that they can be modified with ease by the user whenever their requirement is not met. Along with that one set of the keys based on their requirement can be connected to digital media where on the other side the teacher will mentor all musical notes played by the students. Below are the objectives for this work:

- To build an adjustable piano with its keys detachable/attachable.
- To transmit real-time data from the piano with a recording option.
- To create a virtual music tutorial platform connected to 'dynamic keys piano'.
- To develop and fabricate the detachable key piano circuit at an affordable cost

Different frequency sounds can be produced with the help of a capacitor connected to a transistor based on charging/discharging time constants. By making stretchable cylindrical rods as the base of a piano and making a combined pack of the particular resistors, capacitor, and transistor, to be fixable on the cylindrical rods, piano keys can be made attachable/detachable. The base of the piano consists of 3 main rods i.e. for power supplies and audio output, and 8-bit bus rods for transmitting data to the cloud or any external devices. The core of each key consists of 2 transistors, 8 resistors, and 4 capacitors to adjust frequency along with a clipping mechanism to fit on base rods. The 8-bit unique binary sequence is provided for each key package. When we press the key, respective data is sent to the cloud via a controller (Node MCU ESP8266) along with its notation info, real-time with recording. Using this data in a graphical way, learners, as well as composers, can learn in duplex communication.

## 2. METHODOLOGY

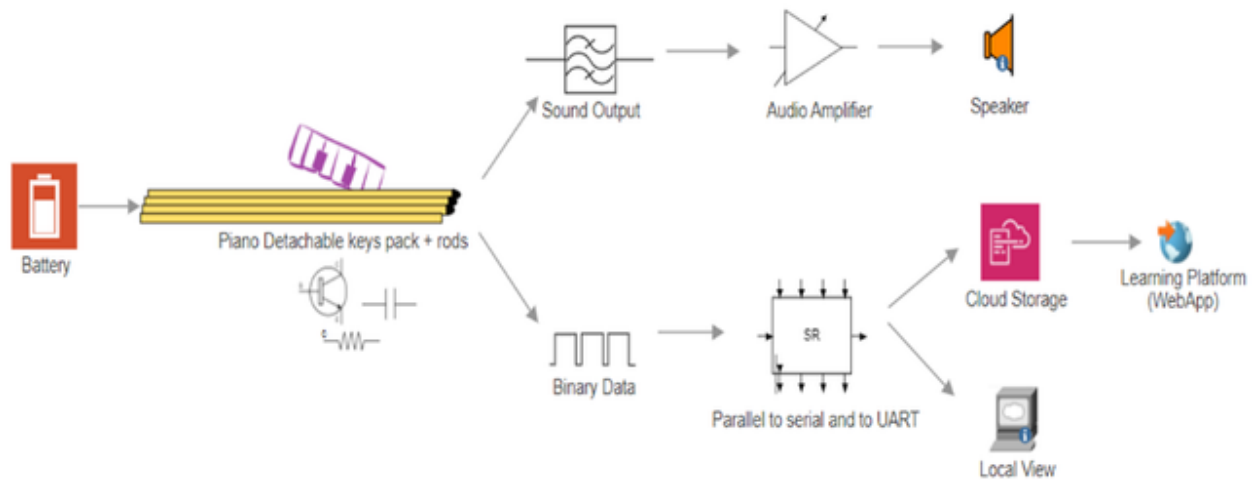


Fig.1 Methodology

- Different frequency sounds can be produced with the help of a capacitor connected to a transistor based on charging/discharging time constants.
- By making stretchable cylindrical rods as the base of a piano and making a combined pack of the particular resistors, capacitors, and transistors, to be fixable on the cylindrical rods, piano keys can be made attachable/detachable.
- The base of the piano consists of 3 main rods i.e., for power supplies and audio output, and 8-bit bus rods for transmitting data to the cloud or any external devices.
- The core of each key consists of 2 transistors, 8 resistors, and 4 capacitors to adjust frequency along with a clipping mechanism to fit on base rods.
- The 8-bit unique binary sequence is provided for each key package.
- When we press the key, respective data is sent to the cloud via a controller (Node MCU ESP8266) along with its notation info, real-time with recording.
- Using this data in a graphical way, learners, as well as composers, can learn in duplex communication.

## 3. THEORY

Detachable keys piano duplex tutor can be mainly divided into the following sub-modules.

1. **Oscillator Circuit:** This is responsible for the different frequency sound generation. Here 2 transistor oscillator models produce the variable, stable frequency output based on the value of the variable capacitance which acts as a time constant controller for the oscillator. The output of this oscillatory circuit is mainly taken out as local sound output. This circuit is an element of a key package
2. **Bus rod connected Switching Key Package (BSKP):** This forms the hardware base for the piano. Here the keys made with the help of different frequency oscillators are packed to form a key package with a U clip hold mechanism. Here 2 in-out ports form the power supply for the key package, and 8 output ports form the binary data output from the package, which will be used for cloud data transmission. U clip hold arrangement ensures

keys fit on the base of the piano, i.e., cylindrical rods which include 8 rods as a data bus and 2 rods for power, and 1 as an output rod.

3. **Opamp amplifier:** The initial output from the piano is of lower amplitude which is barely audible. So, there we use an opamp which is connected with the output from the piano and the final output is the amplitude enhanced signal, resulting in loud and audible sound. Opamp-based amplifiers ensure a gain of around 200.
4. **Cloud Data Uploader:** This module connects the local piano output to the internet. Here the binary data obtained from the key package parallelly is converted to serial data and uploaded to cloud storage along with the conversion data from binary bit to musical notes. It forms the data backend for the duplex tutor platform.
5. **Real-Time Virtual Analyzer:** The notes played by the trainee should be monitored by the trainer so that the learner could get the best output for his efforts. So, whenever the note that is played by the student is wrong, the mentor can correct it then and there and the student can rectify the problem without any delay. This kind of virtual analyzer does not require high bandwidth to transmit binary data. So, it solves time lag problems that have been observed through digital media for teaching.

## 4. DESIGN AND IMPLEMENTATION

The complete design of this detachable keys piano can be subdivided into physical-hardware piano construction and the digital hardware-connected duplex tutor.

### 1. Detachable Keys Piano Base:

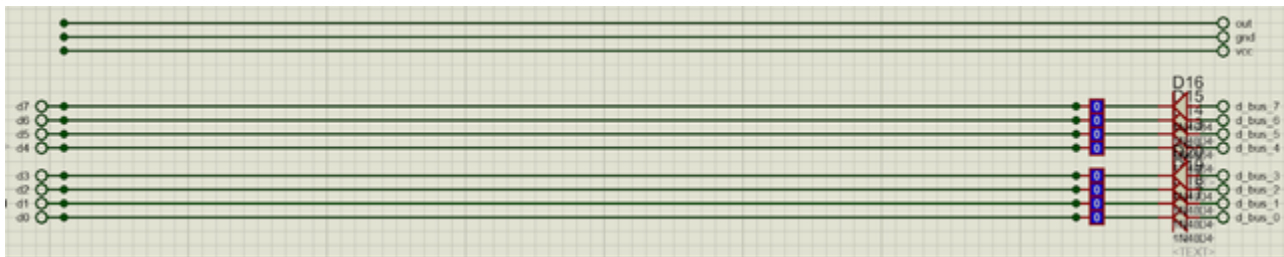


Fig.2 Detachable Keys Piano Base

- It mainly consists of the following:
  - 8 bus rods for binary data transmission (B0 to B7)
  - Diode for each rod to prevent the reverse flow of current back to the key package
  - 3 rods for:
    - Output
    - VCC
    - Ground
  - These are cylindrical rods with a diameter of 0.5cm.
  - These rods can be stretched or compressed based on the requirement of the size of the piano.
  - These rods act as the base for the key package which has to be placed on it through the clip arrangement.

## 2. Key Package

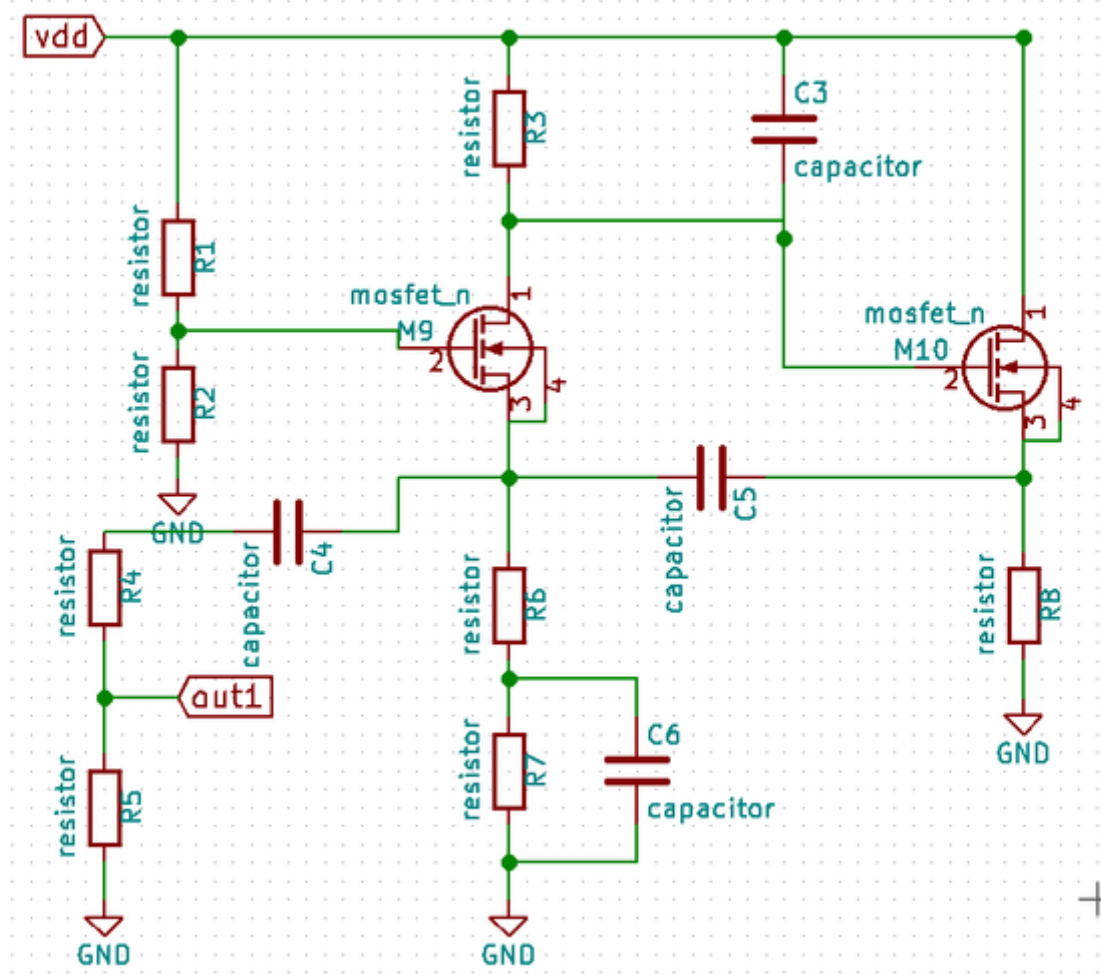


Fig.3 Key Package designed using ESim-KiCad

- The Key Package forms individual buttons on the piano.
- This has to be attached to the base through the clip-hold arrangement.
- This package takes the power supply from the base rods and on the switch press, it will generate the frequency signals.
- These frequency signals again pass through the base rod called “out” of the piano which is connected to the speaker via an amplifier.
- Each key package even outs the binary bit data which is unique for a key. Each key package consists of the following:
  - Pair of NMOS
  - Resistors - 120k,10k(3),6k,1k(2),6.8k
  - Capacitors - 100n,0.5n,5.1n, variable
- Here, the transistors M9 and M10 form the oscillator circuit, and its oscillation frequency is controlled by the charging constant of the capacitor C5.
- C3 is kept constant to maintain the M10 transistor in the saturation region.
- Output is taken across the voltage divider junction at a node between R4 and R5.
- Based upon the value of the capacitor C5, the oscillation frequency changes.

- DC Analysis of the oscillator key package ensures that to keep the transistor in the oscillatory phase and to maintain saturation, 5v is sufficient.
- While carrying out DC Analysis of BJT circuits,
  - Capacitors act like an open circuit. ( $f=0$ ,  $X_C=\infty$ )
  - Inductors act like a short circuit ( $f=0$ ,  $X_L=0$ )
- The below waveform shows the Transient Analysis of the circuit for a variable capacitor value of 120nF.
- The frequency of the generated waveform is around 440 Hz with an amplitude of around 200mV for a 5-volt input supply by using nmos pair (sky130pdk) and around 36mv by using bc547bp transistors pair in place of nmos

#### Construction and Simulation using Esim and Sky130 pdk:

- Construction of this key package is done using Esim and Sky130 pdk is used for its components.
- Simulation is done using ngspice

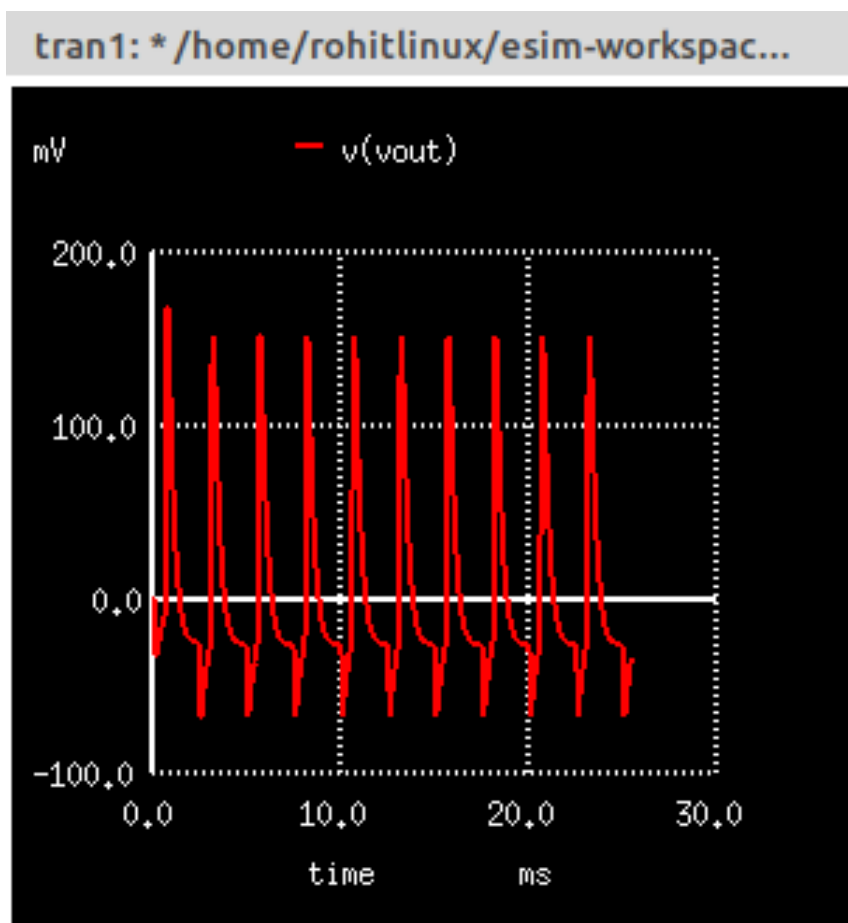


Fig.4 oscillator - transient analysis -ngspice

```

Initial Transient Solution
-----

Node                                Voltage
----                                -
sky130_fd_pr__esd_nfet_05v0_nvt.pm3 0
                                         0
net-_c1-pad2_                        4.54945
net-_m1-pad2_                        1.16279
net-_c2-pad1_                        0.495608
vdd                                   5
net-_c3-pad1_                        3.52725
net-_c4-pad1_                        0.450553
net-_c2-pad2_                        0
vout                                  0
vdd#branch                           -0.000680048

Reference value : 2.48732e-02
No. of Data Rows : 255008

```

Fig.5 oscillator - transient analysis report -ngspice

**Spectrum analysis of the output is done using proteus :**

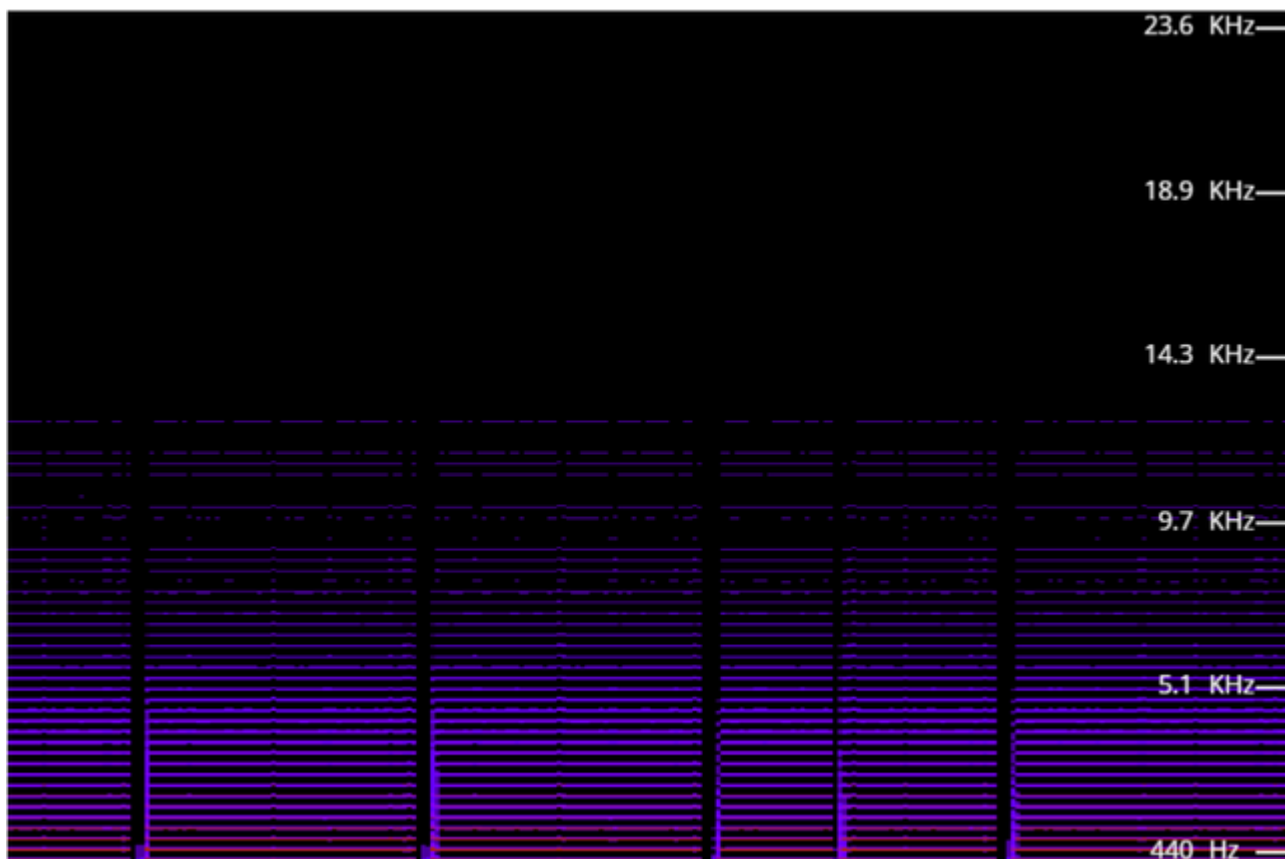


Fig.6 oscillator - spectrum analysis -proteus

### 3. Opamp Amplifier

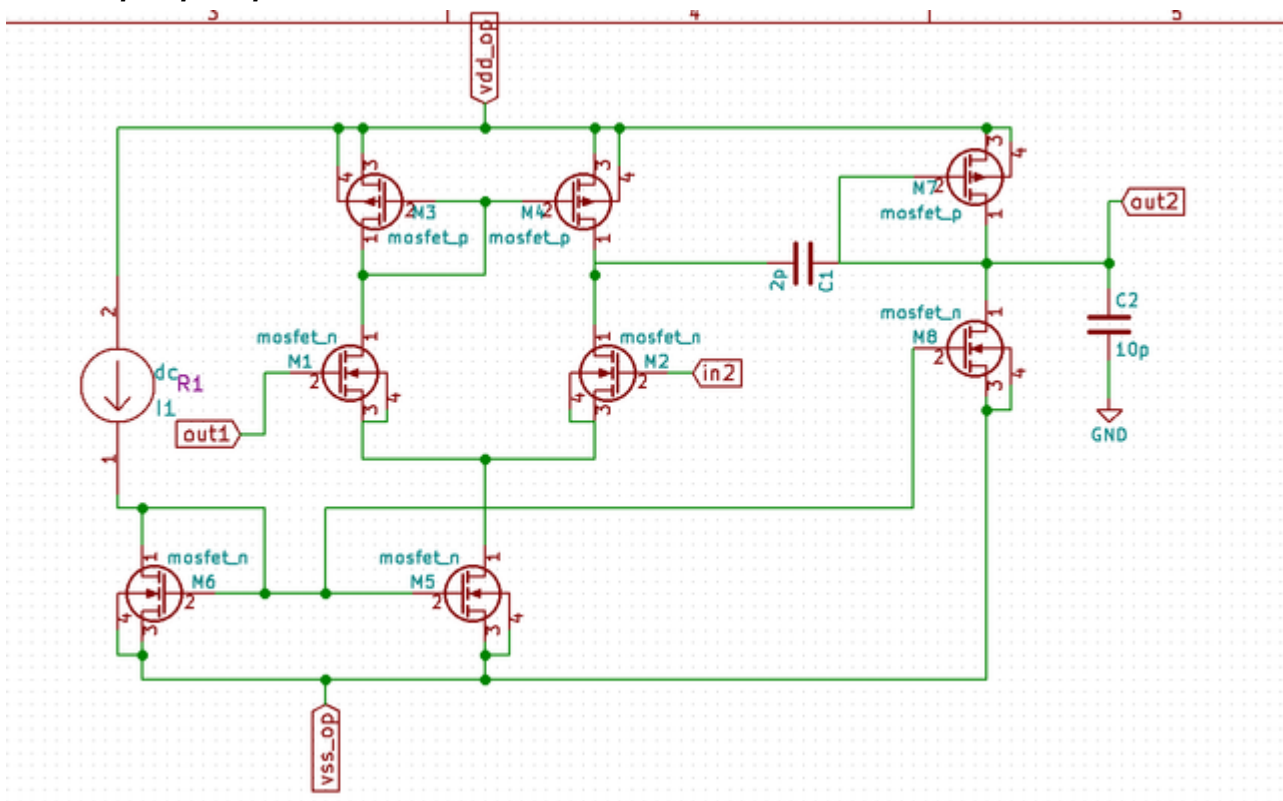


Fig.7 Opamp Amplifier designed using Esim-KiCad

- To amplify the output of the oscillator circuit, a Two-Stage CMOS Operational Amplifier using SkyWater 130nm Technology is used
- It has an NMOS differential amplifier followed by a PMOS Common Source Amplifier to provide a gain of around 40dB.
- The output from the differential pair is taken as single-ended.
- This single-ended output is fed to PMOS common source amplifier
- This opamp is biased using the constant current source of 10uA.

#### **Spice Code (sky130 open-source pdk)**

\* /home/rohitlinux/eSim-Workspace/opamp5.cir

.lib "skywater-pdk-libs-sky130\_fd\_pr/models/sky130.lib.spice" tt

\*oscillator

xM9 Net-\_C3-Pad2\_ Net-\_M9-Pad2\_ Net-\_C4-Pad1\_ Net-\_C4-Pad1\_ sky130\_fd\_pr\_\_nfet\_01v8  
L=1 W=20

xM10 vdd Net-\_C3-Pad2\_ Net-\_C5-Pad1\_ Net-\_C5-Pad1\_ sky130\_fd\_pr\_\_nfet\_01v8 L=1 W=20

R3 vdd Net-\_C3-Pad2\_ 10k

R6 Net-\_C4-Pad1\_ Net-\_C6-Pad1\_ 1k

R7 Net-\_C6-Pad1\_ GND 10k

R8 Net-\_C5-Pad1\_ GND 6.8k

R4 Net-\_C4-Pad2\_ out1 6k

R5 out1 GND 1k  
R1 vdd Net-\_M9-Pad2\_ 33k  
R2 Net-\_M9-Pad2\_ GND 10k

C3 vdd Net-\_C3-Pad2\_ 5.1n  
C5 Net-\_C5-Pad1\_ Net-\_C4-Pad1\_ 110n  
C4 Net-\_C4-Pad1\_ Net-\_C4-Pad2\_ 100n  
C6 Net-\_C6-Pad1\_ GND 0.5n

\*Opamp

xM1 Net-\_M1-Pad1\_ out1 Net-\_M1-Pad3\_ Net-\_M1-Pad3\_ sky130\_fd\_pr\_\_nfet\_01v8 l=1 w=1.79

xM2 Net-\_C1-Pad2\_ in2 Net-\_M1-Pad3\_ Net-\_M1-Pad3\_ sky130\_fd\_pr\_\_nfet\_01v8 l=1 w=1.79

xM3 Net-\_M1-Pad1\_ Net-\_M1-Pad1\_ vdd\_op vdd\_op sky130\_fd\_pr\_\_pfet\_01v8 l=1 w=10

xM4 Net-\_C1-Pad2\_ Net-\_M1-Pad1\_ vdd\_op vdd\_op sky130\_fd\_pr\_\_pfet\_01v8 l=1 w=10

xM5 Net-\_M1-Pad3\_ Net-\_I1-Pad1\_ vss\_op vss\_op sky130\_fd\_pr\_\_nfet\_01v8 l=1 w=20

xM6 Net-\_I1-Pad1\_ Net-\_I1-Pad1\_ vss\_op vss\_op sky130\_fd\_pr\_\_nfet\_01v8 l=1 w=20

I1 Net-\_I1-Pad1\_ vdd\_op dc 10u

xM7 out2 out2 vdd\_op vdd\_op sky130\_fd\_pr\_\_pfet\_01v8 l=1 w=62.83

xM8 out2 Net-\_I1-Pad1\_ vss\_op vss\_op sky130\_fd\_pr\_\_nfet\_01v8 l=1 w=62.83

C1 out2 Net-\_C1-Pad2\_ 2p

C2 out2 GND 10p

v1 vdd GND DC 5

v5 in2 GND 0

v3 vdd\_op GND DC 4

v4 vss\_op GND DC -4

\*Simulation Command

.tran 0.1us 25500us

\* ngspice control statements

.control

run

\*For Transient Analysis

\*Oscillator Out

plot v(out1)

\*Opamp out

plot v(out2)

.endc

.end



#### 4. Binary Data Handler

- The key package along with the data produces the binary information which is unique for each key.
- For an 8-bit data bus, the total number of unique binary patterns will be  $2^8 - 1$ . i.e., 255 unique combinations exist excluding 0000\_0000 which represents no key is pressed.
- These parallel bit data are uploaded to the firebase real-time database using an esp8266 Wi-Fi module (node MCU). Binary data bits are converted to the corresponding musical notations.

#### 5. Duplex Tutor Platform

- This is the digital web interface of the hardware piano from the real-time database.
- Buttons pressed on the hardware piano will directly reflect here.
- There will be a separate channel for a predefined set of detachable keys piano and a duplex tutor.
- It helps in advancing the learning of the piano for beginners.
- Both the learners and composers can interact in the most efficient way.
- For each individual duplex piano platform, there will be login credentials, learners and composers have to log in to this portal along with the specified hardware. On successful login, the user will be redirected to the learning platform.



Fig.8.Learning Platform

### 5. DEMO

For the demo, proteus is used since it requires an Internet connection to upload data from the circuit to the cloud.

<https://www.youtube.com/watch?v=aoMrV8k0poE>

(In this video, specific transistors are used, in the schematic download files, these are replaced by NMOS)

For the below section please see/download from:  
<https://github.com/ROHITDH/Detachable-Keys-Piano>

## 6. DOWNLOAD

- eSim: Schematic File
- ngspice: Spice Code using Sky130pdk File
- LtSpice Files
- Proteus File
- Node MCU, and Arduino Data Uploader Files
- Literature survey
- Report
- Demo Video
- WebApp Interface      Requires Hardware/Proteus Files

## 7. TOOLS USED

- eSim EDA Tool
- SkyWater SKY130 PDK
- LTspice
- ngspice